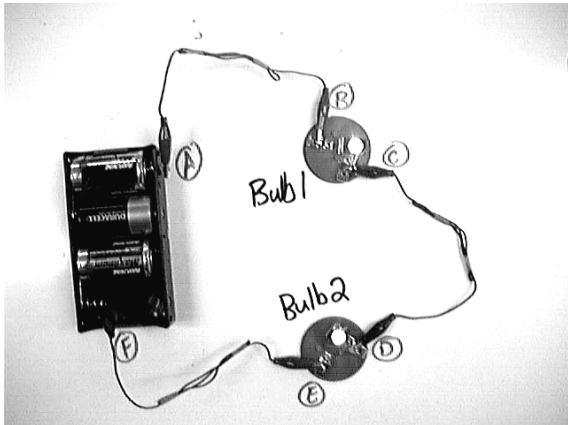


# Unit 11 - Activity 1



## Prediction:

Point	Bulb 1 Lit / Unlit	Bulb 2 Lit / Unlit
A		
B		
C		
D		
E		
F		

What will happen to bulbs 1 and 2 when you disconnect the wires at various points?

## Observation(s):

Point	Bulb 1 Lit / Unlit	Bulb 2 Lit / Unlit
A		
B		
C		
D		
E		
F		

Briefly explain your reasoning for point predictions B, D, and E.

### Conclusion:

(Your answer to the focus question in the “V” above.)

### Consensus: