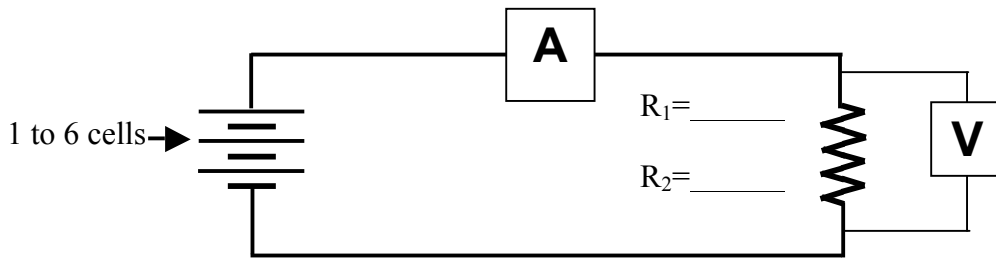


Unit 11 - Activity 10



Prediction

ΔV (V)

I (A)

What is the relationship between voltage and current?

Observation(s)

R_1

cells	ΔV (volts)	I (amps)
1		
2		
3		
4		
5		
6		

R_2

cells	ΔV (volts)	I (amps)
1		
2		
3		
4		
5		
6		

Use Graphical Analysis or Logger Pro to plot data to find the relationship between ΔV and I .

Conclusion:

Consensus:

New Terms: